

Assignment – 8

Design a circuit of ALU. Input will be taken from a memory through register. Perform various operations on input/Instruction. Operations are ADD, ADDI, SUB, OR, NOT. Output will be stored in register.

Input size : 16 bit. Use splitter to split the instruction.